
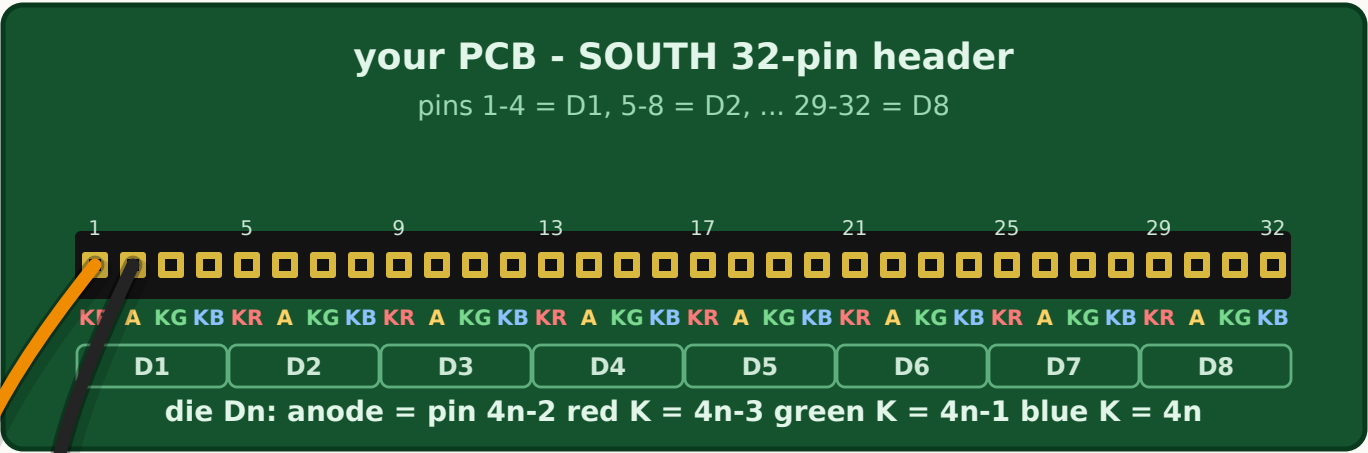


Step 6 - reverse leakage. Rewire from the sweep rig.

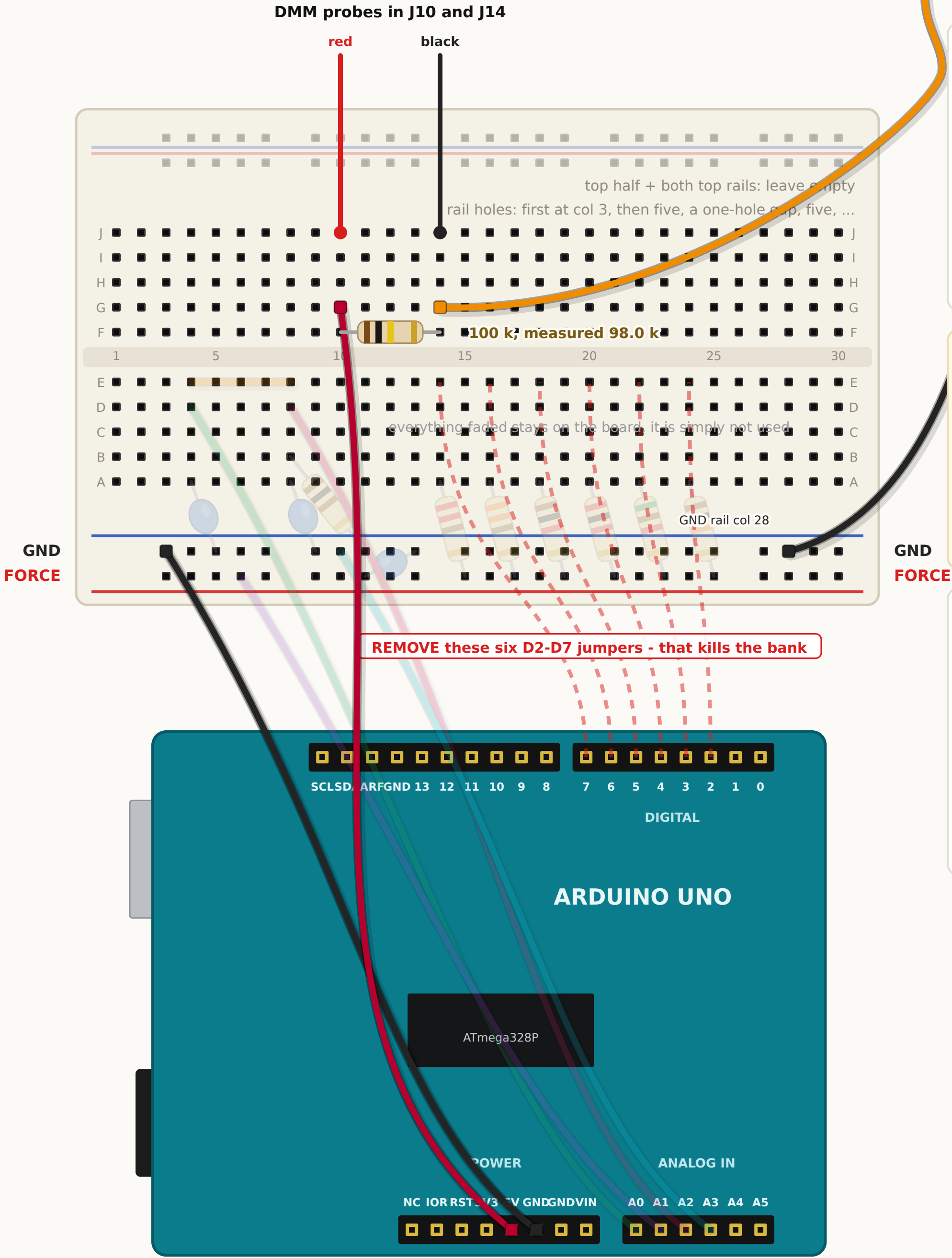Different circuit. The bank comes off, the die is driven BACKWARDS, and the DMM reads across a 100 k resistor.



the rewire, in five moves

- 1 PULL the six jumpers off UNO D2-D7. Bank is dead.
- 2 ADD a jumper: UNO 5V -> G10.
- 3 ADD the 100 k across the top half: F10 to F14.
- 4 MOVE F/M #1 to G14, out to the die CATHODE.
- 5 MOVE F/M #2 to GND rail col 28, out to the ANODE.


reading it

DMM: 2 clicks clockwise from OFF (DC volts), then RANGE down to mV. Red probe on the 5V side of the 100 k. Wait 5 seconds to settle, then read the millivolts.

$$i_{\text{leak}} = V_{\text{mV}} / 98.0 \text{ k} \rightarrow 1 \text{ uA reads } 98 \text{ mV}$$

Red on every die. Green and blue only where round 1 flagged something.

the circuit

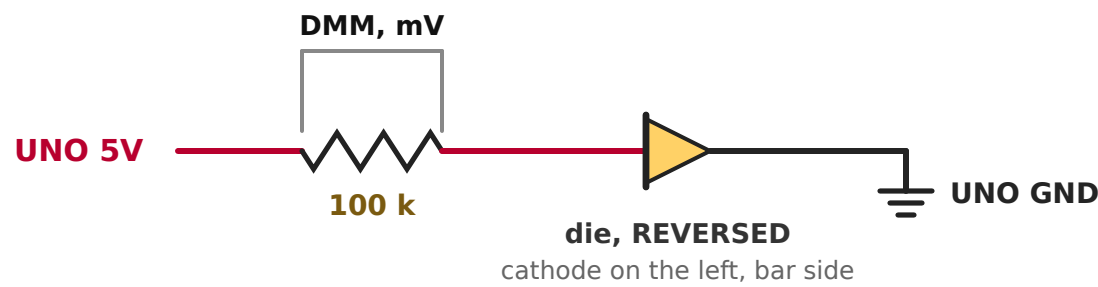

5 V reverse across the die. Never exceed that.

Contact resistance is irrelevant here: nanoamps through 98 k.