
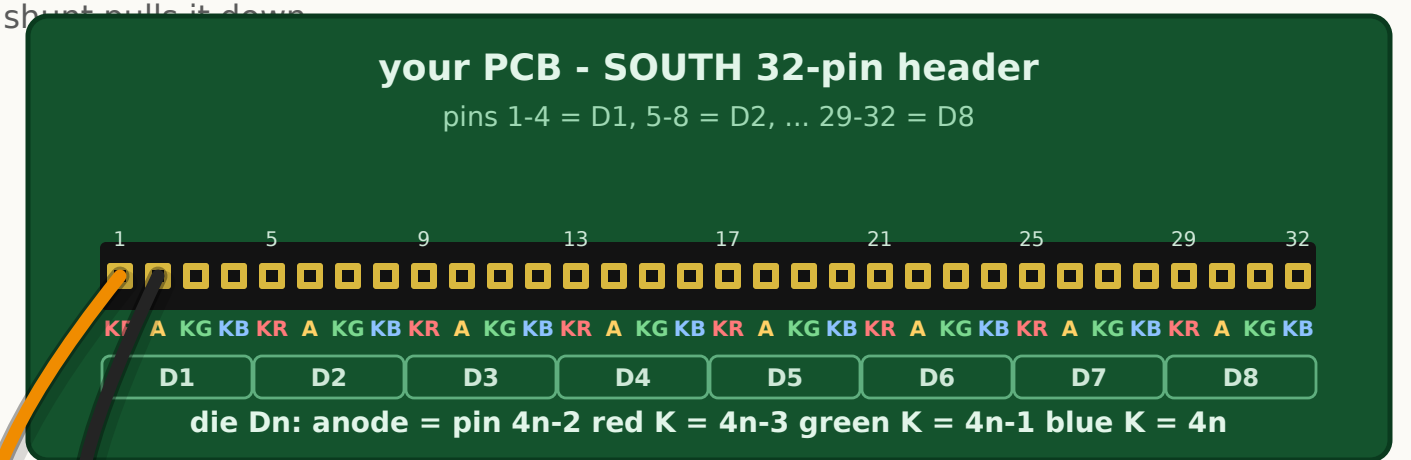


The bank comes off, the die is driven BACKWARDS, and the meter reads ACROSS THE DIE. Healthy reads near 5 V; a short pulls it down

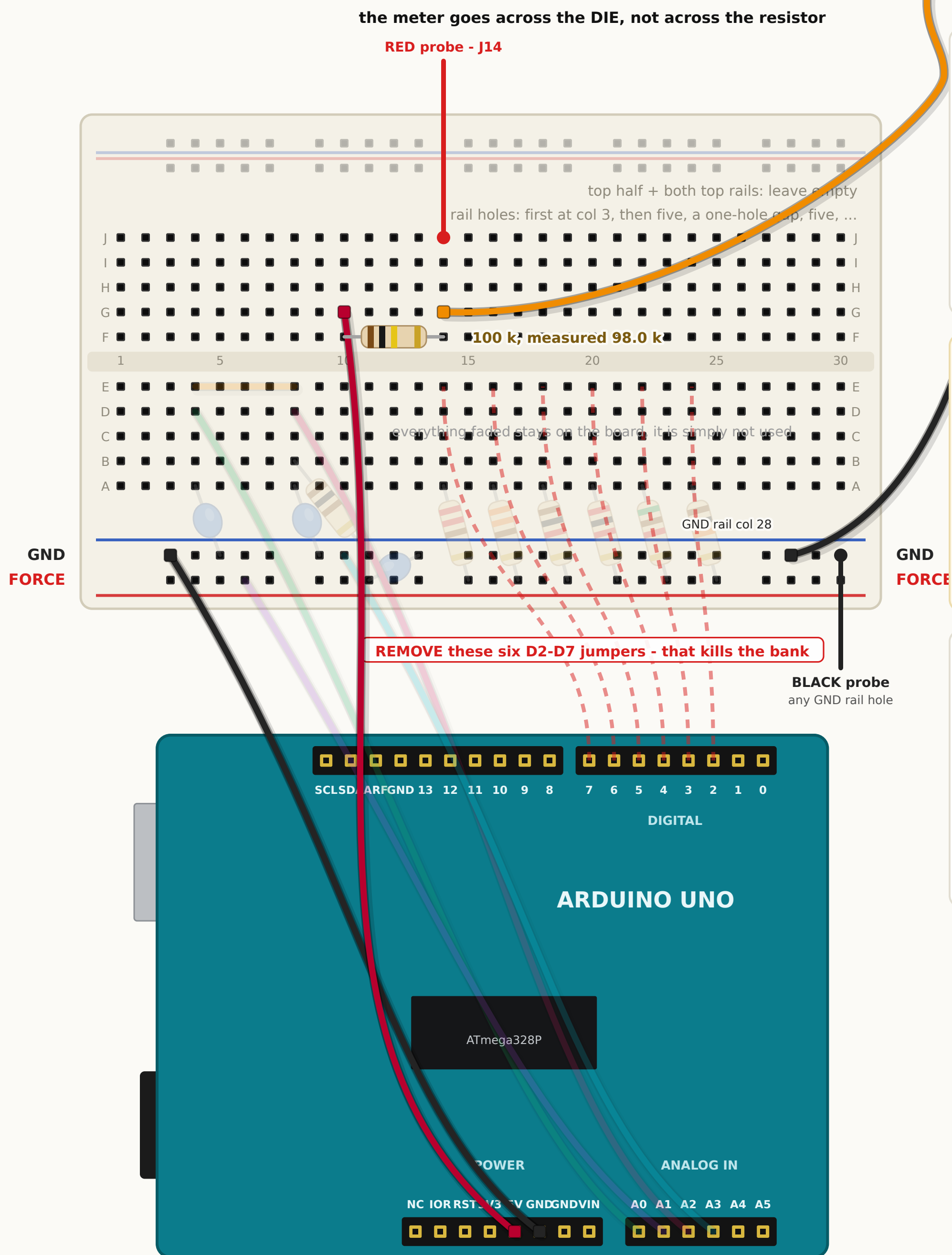The bank comes off, the die is driven BACKWARDS, and the meter reads ACROSS THE DIE. Healthy reads near 5 V; a short pulls it down



the rewire, in five moves

- 1 PULL the six jumpers off UNO D2-D7. Bank is dead.
- 2 ADD a jumper: UNO 5V -> G10.
- 3 ADD the 100 k across the top half: F10 to F14.
- 4 MOVE F/M #1 to G14, out to the die CATHODE.
- 5 MOVE F/M #2 to GND rail col 28, out to the ANODE.


reading it

DMM on DC VOLTS, 20 V range. Not millivolts.
Red probe in J14, black in any GND rail hole.
Wait 5 seconds, then read the volts.

healthy die (>10 M) about 4.95 V
1 M shunt 4.50 V
100 k shunt 2.49 V
2.9 k shunt 0.14 V

Low reading = a conducting path around the junction.

the circuit

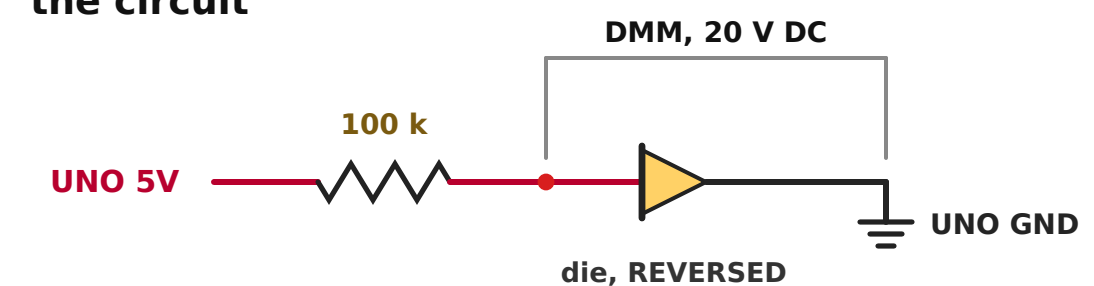

The 100 k and the die form a divider off the 5 V rail. The die's own resistance sets the reading.

5 V reverse maximum. Never exceed it.